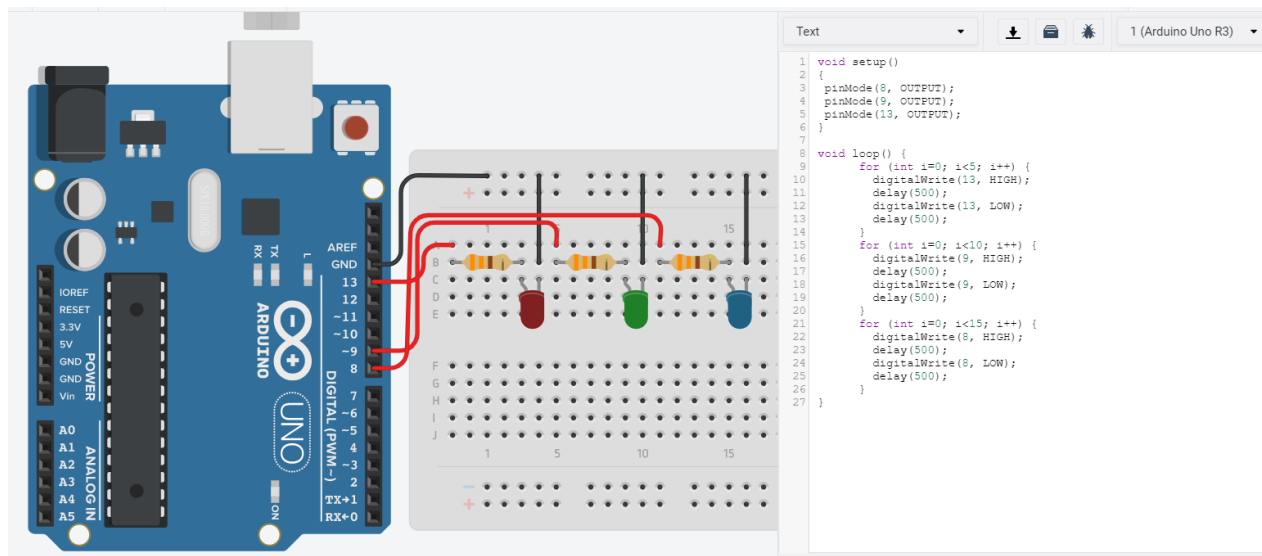


Arduino Tutorial 3: Understanding How Breadboards Work

Watch the video: <https://www.youtube.com/watch?v=CfdaJ4z4u4w>

Build the circuit as outlined in the video. Take a picture of your circuit and post it below.
Level 4: Proper wire colours, resistor values, no two wires in the same pin, screen capture of arduino and code only (not entire screen), works

SCREEN CAPTURE



Bonus: Build the following circuit. Get the LED to light by adding more wires. You are not

allowed to add wires within the black circle. Your LED should not explode!



=BAD

You can replace the picture with your solution.

